




Binary multiplier

It multiplies 2 binary numbers of multiplier and multiplicand


2 bit by 2 bit multiplier

If no. of digits in
multiplicand &
multiplier = i, j

Max. no. of bit
of O/P = $i+j$

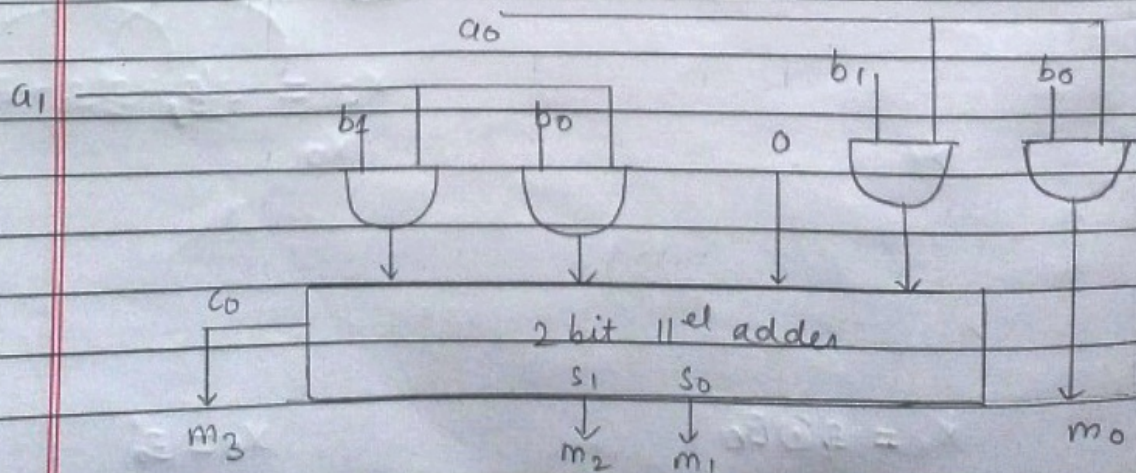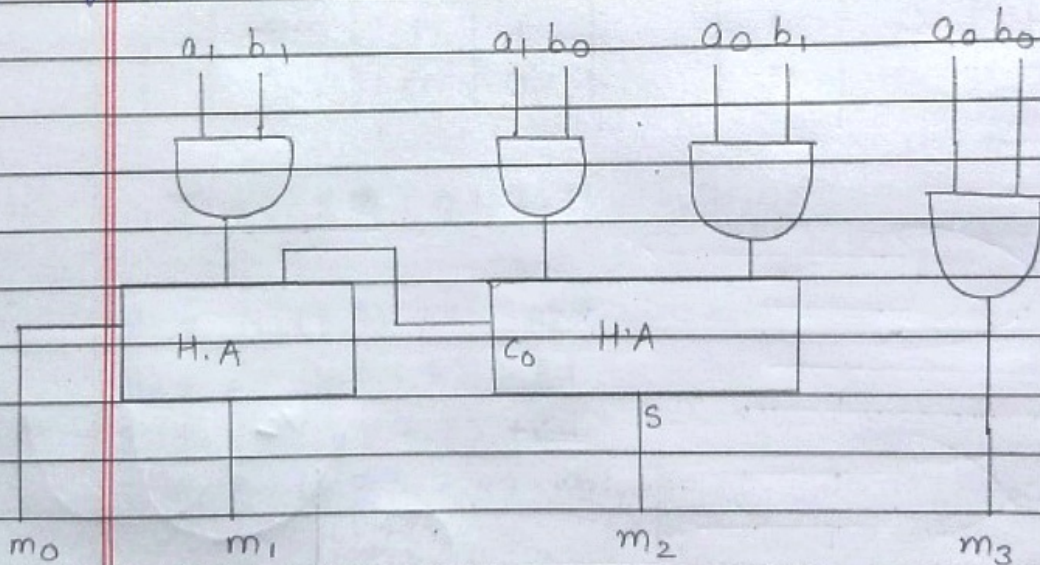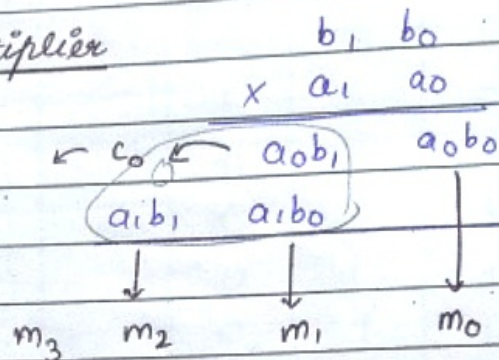

4 bit by 3 bit multiplier

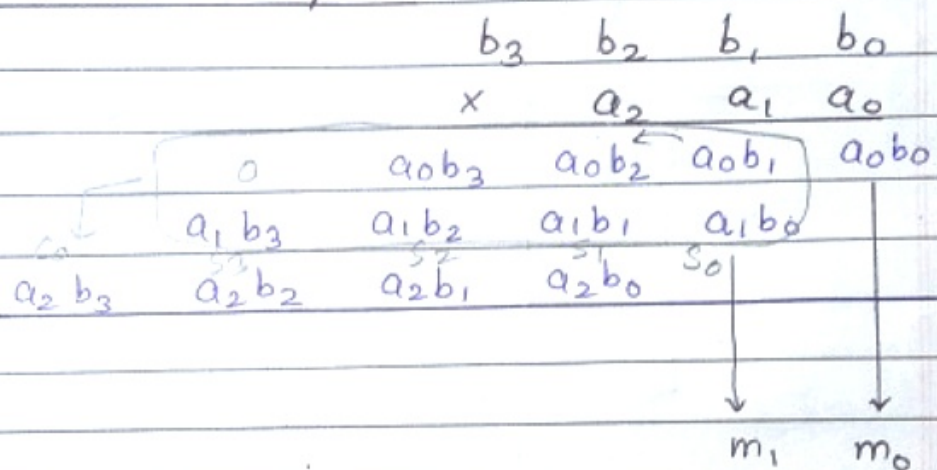

NOTE: If size of 1st number is 'i' and 2nd number is 'j'.

then, total AND gates = $i * j$

total parallel adder = $(2^i - 1)$ of i bit

